

Analog Lab (EE2401)

Experiment 5 : Voltage controlled oscillator

EE19BTECH11041,
Srijith Reddy Pakala
Department of Electrical Engineering
IIT Hyderabad

March 4, 2021

1 Aim

Understand the operation of a schmitt trigger based oscillator.

Design a variable frequency oscillator controlled by voltage.


Schmitt trigger

A Schmitt trigger is a comparator circuit with hysteresis implemented by applying positive feedback to the noninverting input of a comparator or differential amplifier.

2 Problem statement

 
1. Design a schmitt trigger based oscillator with the following specifications:

- . • Oscillation frequency: 10 kHz.
- . • Hysterisis width for schmitt trigger: Around 20 % of the opamp peak-to-peak output swing.
- . • LF347 opamp with +5V/-5V dual supply.



 2. Below is a modified oscillator with a control voltage (V_C) input to vary the oscillation frequency. Here, V_C decides the rate of integration and hence controls the output frequency. Transistor Q_1 introduces an inversion, therefore the schmitt trigger is also inverting. R_B is for controlling the base current of Q_1 and D_1 protects the transistor from breakdown during negative swing. :


- . • Analyze and calculate component values assuming Q_1 to act like an ideal switch.
- . • frequency 10-15 kHz for V_C ranging from 4-6 V.
- . • Generate $V_C/2$ from V_C using a voltage divider.
- . • Q_1 : 2N3904, D_1 : 1N4148
- . • Plot frequency vs V_C characteristics. Is it expected?



3. Change R or C to obtain new frequency range of 100-150 kHz for the same V_C range as above. Plot frequency vs V_C . Is it linear? Explain. In reality Q_1 doesn't act like an ideal switch. It has a saturation voltage of around 0.2 V. This can cause deviation in the expected duty cycle. Modify the circuit in Problem 2 to compensate this effect. You can assume a matched transistor is available.


3 Analysis and simulation

Question1

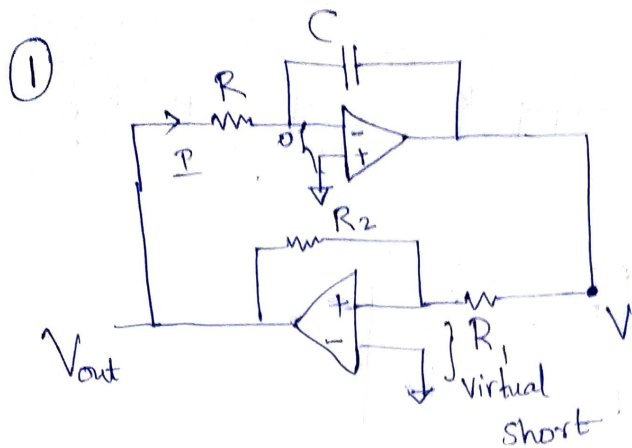

Given hysteresis width is 20% of peak to peak opamp.
 
$$\Rightarrow V_e = \frac{V_{out} R_1 + V_1 R_2}{R_1 + R_2}$$



At $V_e = 0$, $2V_1$ is hysteresis width

$$\Rightarrow V_e = 0 = \frac{V_{out} R_1 + V_1 R_2}{R_1 + R_2}$$

$$\Rightarrow V_1 = -\frac{V_{out} R_1}{R_2}$$

①

$$\Rightarrow V_1 = \frac{\text{op-amp peak}}{5} = \frac{\text{op-amp peak } R_1}{R_2}$$

$$\Rightarrow \boxed{R_1 = \frac{R_2}{5}}$$

$$V_1 = - \int \frac{V_{\text{out}} dt}{RC}$$

Let us suppose $V_e > 0$ at $t=0$ and therefore $V_{\text{out}} = 3.5 = V_{\text{peak}} = V_p$.

then.

$$V_e = \frac{V_{\text{out}} R_1 - \frac{R_2 \int V_{\text{out}} dt}{RC}}{RC}$$

As the capacitor charges V_e will become Zero at $t=t_1$

$$\Rightarrow t_1 = \frac{R_1 RC}{R_2}$$

① Now the actual cycle starts.

when $t > t_1$ $V_e < 0 \Rightarrow V_{out} = -V_p$

$$\Rightarrow V_e = \frac{-V_p R_1 + \frac{R_2 \int_{t_1}^{t_2} V_p dt}{RC} + \frac{R_2 \int_0^{t_1} -V_p dt}{RC}}{R_1 + R_2}$$

$$R_1 + R_2$$

$$\Rightarrow V_e = 0 \bigg|_{t=t_2}$$

$$\Rightarrow \frac{R_2 V_p (t_2 - t_1)}{RC} = 2V_p R_1$$


$$\Rightarrow \Delta t = t_2 - t_1 = \frac{2RC R_1}{R_2}$$

Here Δt is half the Time period.

$$\Rightarrow T = 2\Delta t = \frac{4RC R_1}{R_2} = \frac{4RC}{5}$$


$$\boxed{f = \frac{5}{4RC}}$$

Schematic

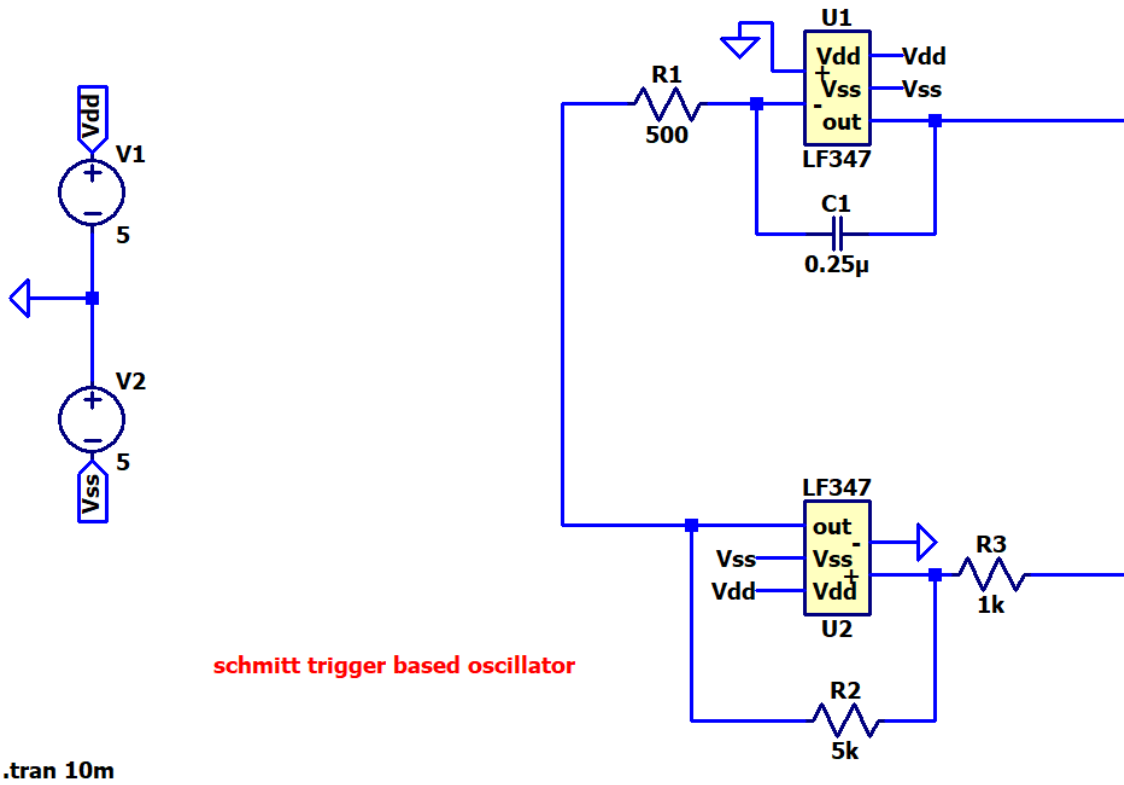


Circuit schematic

Output

 


- As we can see the frequency is 9.4KHz which is deviated from the expected value 10KHz and duty cycle here is 50.0157%.
- The may be accounted by the non ideal characteristics of opamp we used .

Question2

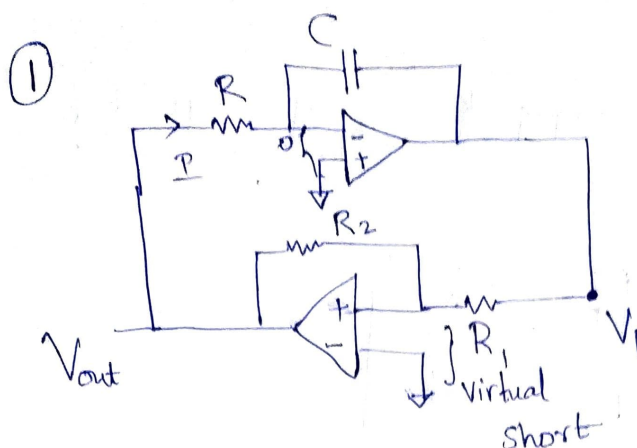

Given hysteresis width is 20% of peak to peak opamp.
 
$$\Rightarrow V_e = \frac{V_{out} R_1 + V_1 R_2}{R_1 + R_2}$$



At $V_e = 0$, $2V_1$ is hysteresis width

$$\Rightarrow V_e = 0 = \frac{V_{out} R_1 + V_1 R_2}{R_1 + R_2}$$

$$\Rightarrow V_1 = -\frac{V_{out} R_1}{R_2}$$

(2)

$$V_e = \frac{V_{out} R_1}{R_1 + R_3} - V_1$$

Similarly using 20% peak hysteresis

$$\frac{R_1}{R_1 + R_3} = \frac{1}{5}$$

$$\Rightarrow R_3 = 4R_1$$

$$V_1 = \frac{V_c}{2} - \int \frac{V_c}{2RC} dt, \quad V_e > 0, V_{out} > 0$$

$$V_1 = \frac{V_c}{2} + \int \frac{V_c}{2RC} dt, \quad V_e < 0, V_{out} < 0$$

Now let's say at $t=0$ $V_e > 0$ and cap is uncharged. $\Rightarrow V_{out} = V_p$

$$V_e = \frac{V_{out} R_1}{R_1 + R_3} + \int_0^t \frac{V_c}{2RC} dt - \frac{V_c}{2}$$

As cap charges $V_e \downarrow$ and at $t=t_1, V_e = 0$

$$\Rightarrow 0 = \frac{V_c}{2} \left(\frac{t_1}{RC} - 1 \right) + \frac{V_{out} R_1}{R_1 + R_3}$$

(2)

$$t_1 = RC - \left(RC \frac{2V_{out} R_1}{V_c (R_1 + R_3)} \right)$$

Now. At $t > t_1$, $V_e < 0 \Rightarrow V_{out} = -V_p$

Now the actual cycles will start.

let t_2 be t at which $V_e = 0$ when $V_{out} = -V_p$

$$\Rightarrow V_e = \frac{-V_p R_1}{R_1 + R_3} - \int_{t_1}^{t_2} \frac{V_c}{2RC} dt$$

$$= \frac{-V_p R_1}{R_1 + R_3}$$

$$\Rightarrow V_e|_{t=t_2} = 0$$

$$\Rightarrow (t_2 - t_1) V_c = \frac{4RC V_p R_1}{R_1 + R_3}$$

$$\Rightarrow \Delta t = \frac{T}{2} = \frac{4RC V_p R_1}{V_c (R_1 + R_3)}$$

$$\boxed{T = \frac{8RC R_1}{(R_1 + R_3)} \frac{V_p}{V_c}} = \frac{8RC V_p}{5 V_c}$$

$$(2) \quad f = \frac{5V_c}{8RCV_p}$$

Now from simulation $V_p \approx 3.5V$

we need $f = 10KHz \mid V_c = 4V$

$$\Rightarrow \frac{5 \times 4}{8RC(3.5)} = 10KHz$$

$$\Rightarrow R = 1K, C = 35.714nF$$

Now coming to R_B . R_B controls I_B at Q_1 and maintain D_1 from breakdown.


R_B should be higher such that D_1 is safe and lower enough such that

Q_1 is in saturation i.e. $I_B > \frac{I_C}{\beta}$

$$\frac{V_{out} - 0.7}{R_B} > \frac{V_c}{2R\beta}, \text{ Typically } R_B < 100K$$

we choose $R_B = 10K$.

Schematic

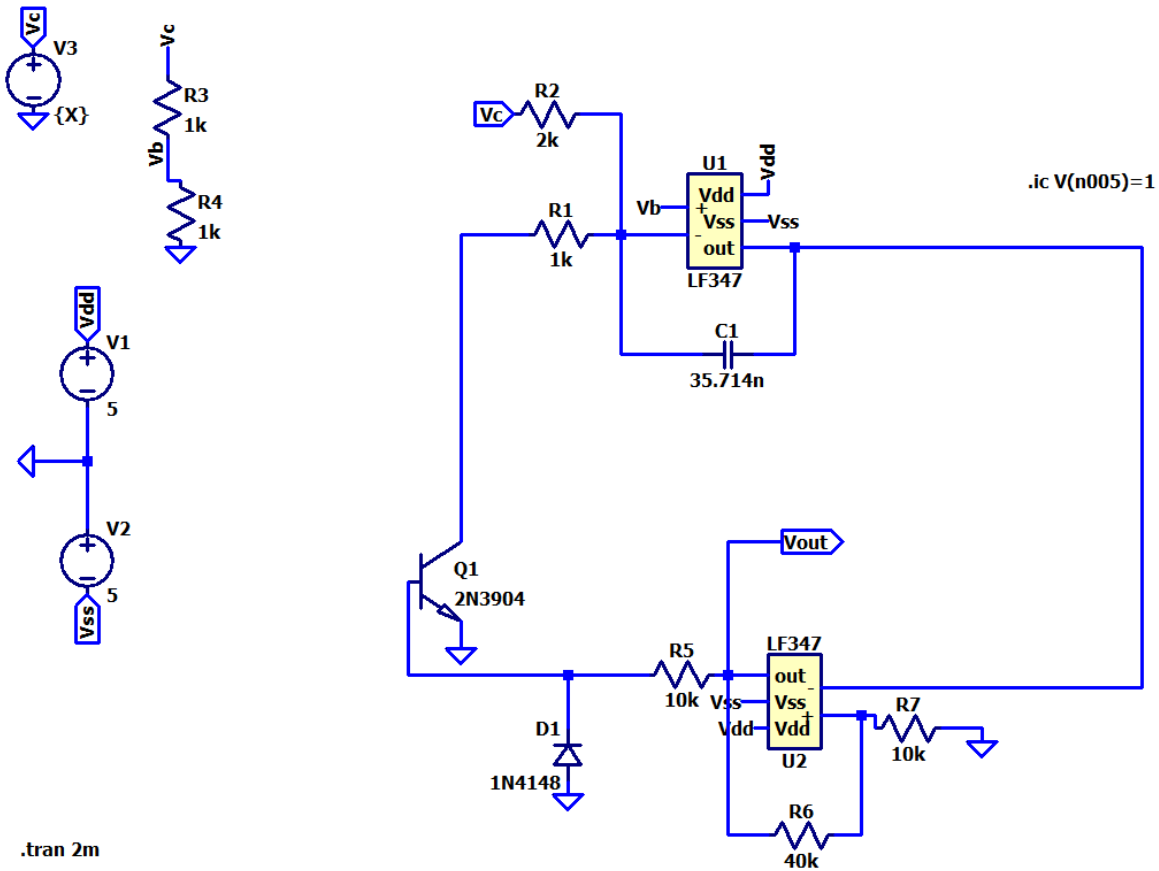


Circuit schematic

```
.step param X 4 6 0.01
```

```
.meas tran T3 find time when V(vout)=0 fall 10
.meas tran T1 find time when V(vout)=0 rise 10
.meas tran T2 find time when V(vout)=0 rise 11
.meas tran Frequency param 1/(T2-T1)
.meas tran duty PARAM (T3-T1)/(T2-T1)
```

- To find frequency as V_C varies we have used above statements and also for duty cycle.


f as V_C varies

 


f Vs V_C

- We can see that the frequency is increasing linearly w.r.t to V_C .
- But similar from the first question the frequency here is also deviated from the expected values.
- The duty cycle here is 50.3009%.

V_{out} at $V_C=5V$

 


Voltage at collector of Q_1

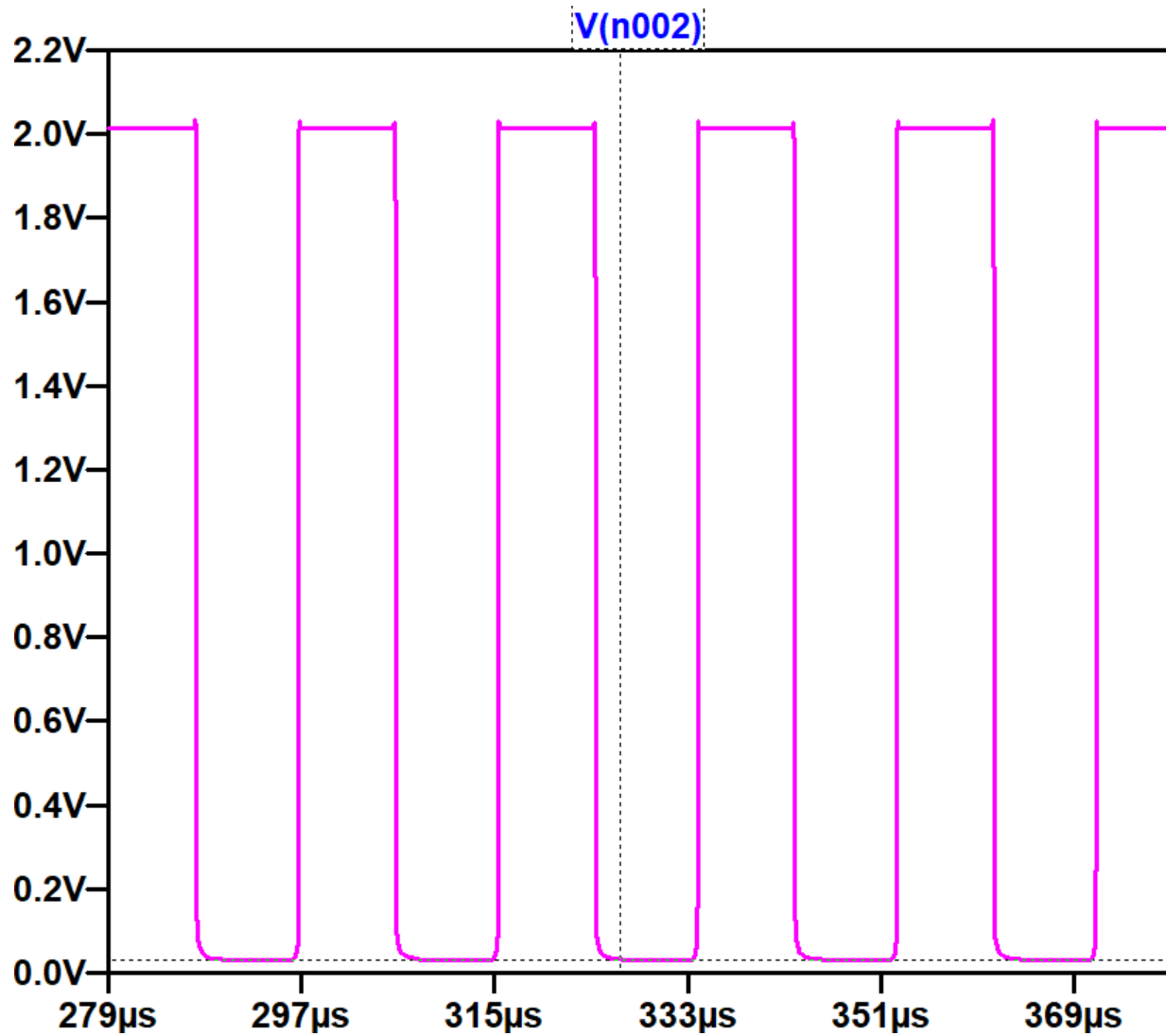

$V_{Collector}$ Vs time(ms)

- From the above plot the saturation voltage is 30mV which is quite low and good for the circuit.


Question3 Schematic

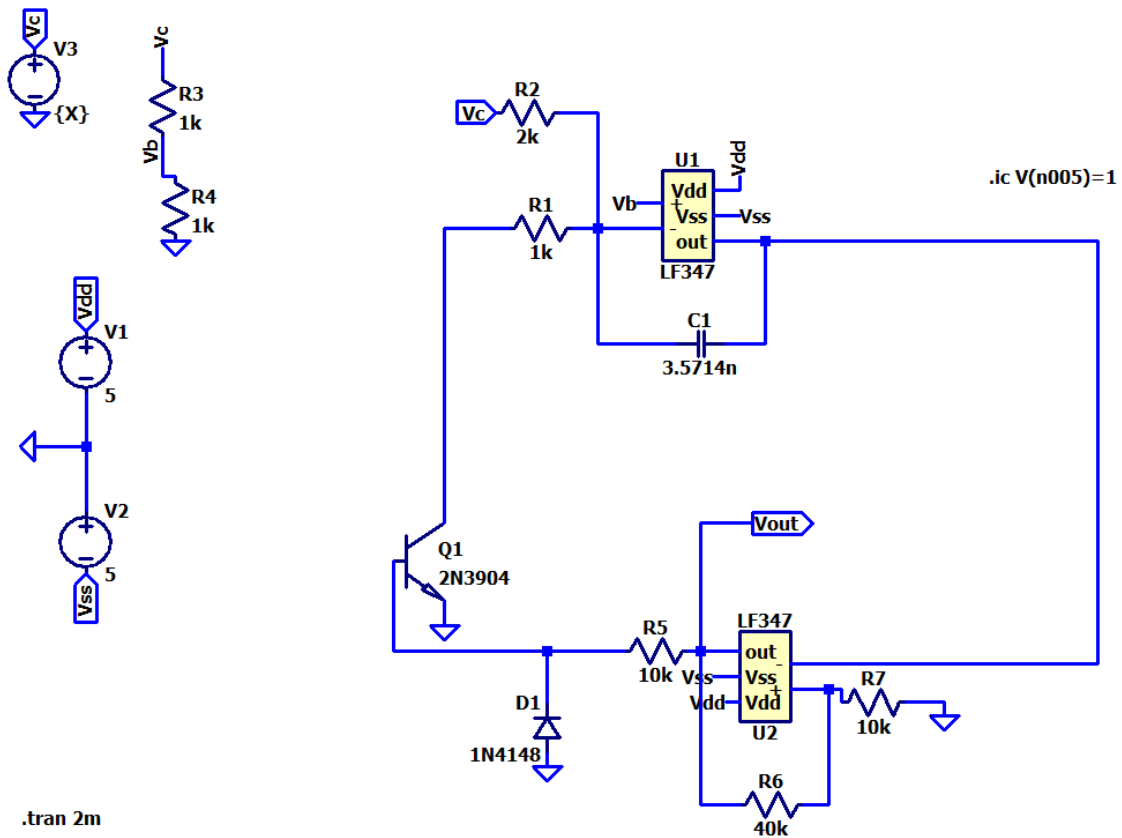

Circuit schematic

- We have changed R and C such that frequency range is 100KHz to 150KHz.

f as V_C varies

 


f Vs V_C

- We can see that the frequency is increasing w.r.t to V_C but non-linear.
- The frequencies observed is very much deviated from the expected value, the reason is that opamp output cannot change faster than slew rate.
- The duty cycle here is 0.511321% at $V_C=6V$.

③ In reality Q_1 is not an ideal Switch so, to we need to compensate its saturation effect.



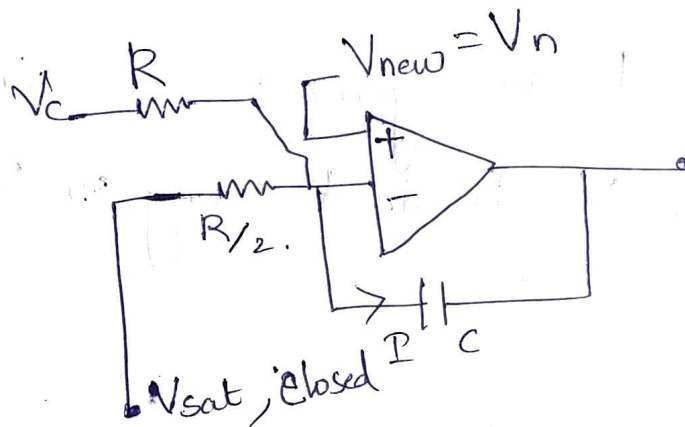we can change non-inverting input of integrator such that, current through capacitor has same magnitude.



$$\text{closed} \\ -I_p = \frac{V_c - V_n}{R} - \frac{(V_n - V_{sat})}{R/2}$$

open

$$+I_p = \frac{V_c - V_n}{R}$$

③


$$\Rightarrow \frac{V_C - V_n}{R} = \frac{2(V_n - V_{sat})}{R} - \left(\frac{V_C - V_n}{R} \right)$$

$$\Rightarrow V_C - V_n = V_n - V_{sat}$$

$$\Rightarrow \boxed{V_n = \frac{V_C}{2} + \frac{V_{sat}}{2}}$$

Now we need to generate a circuit such that V_n is obtained using matched transistor.

Method 1:

 

③ Now let's write equations.

$$V_{CE} = V_C - I_C r_C - I_E r_E \quad \text{--- (1)}$$

$$(V_C - I_B r_b - 0.7) = I_E r_E \quad \text{--- (2)}$$

$$I_B = \frac{I_C}{\beta} \quad \text{--- (3)}$$

$$I_E = (\beta + 1) I_B = I_B + I_C \quad \text{--- (4)}$$

$$\Rightarrow V_n = \frac{\beta r_C V_{sat} + (\beta + 1) r_E V_C}{\beta r_C + (\beta + 1) r_E}$$

By comparing $V_n = \frac{V_C}{2} + \frac{V_{sat}}{2}$


$$\beta r_C \neq (\beta + 1) r_E$$

Assuming $\beta \gg 1$

$$\Rightarrow r_C \approx r_E, \quad \underline{r_B \approx \beta r_C}$$


③ Method 2

 Since we don't know we can use this method.




we can use r in the range of $1k$.

Schematic

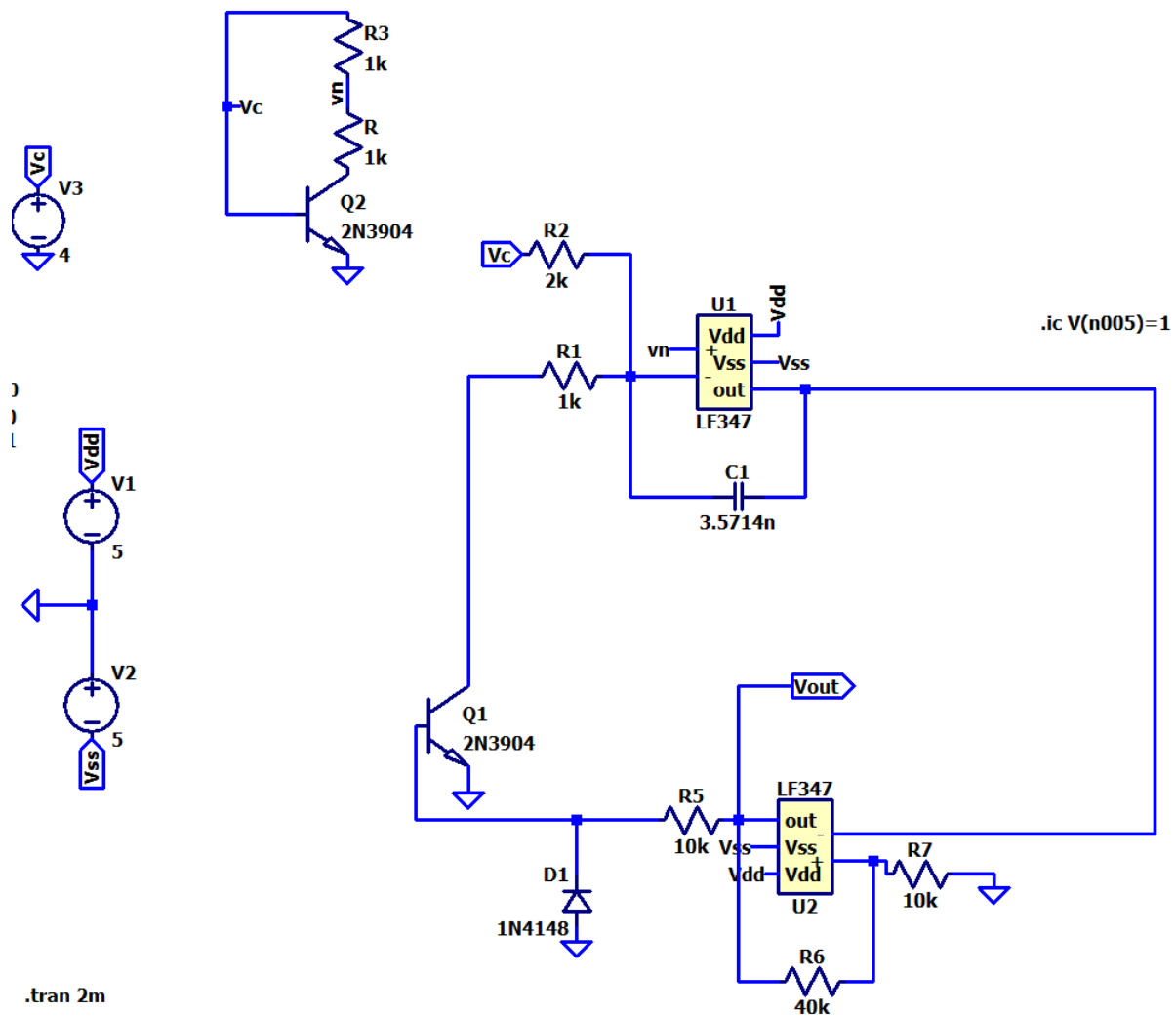

Circuit schematic with compensation

V_{out} at $V_C=4V$

 

- Duty cycle observed here is 0.513224%.
- There is not much of a difference in duty cycle here because of low saturation voltage i.e 30mV. It could be helpful if our saturation would have high.

Thank
you