

Analog Lab (EE2401) Experiment 6 : PCB Design

EE19BTECH11041, Srijith Reddy Pakala

Department of Electrical Engineering
IIT Hyderabad

March 11, 2021

1 Aim

our aim here is to design PCB boards for the voltage controlled oscillator using Kicad.


2 Problem statement

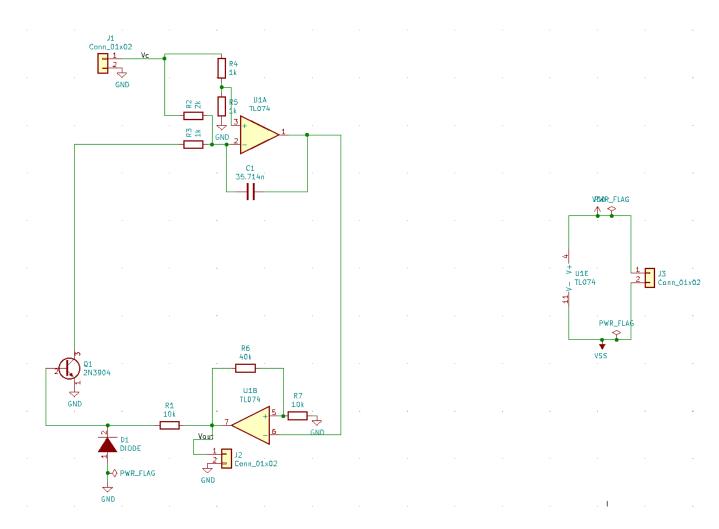- 1. Design a PCB for the voltage-controlled oscillator implemented in Experiment 5.
- . Two layer PCB.
- 2-pin connectors for supply, input and output.
- Use only one TL074 (same symbol and footprint as LF347) IC with four opamps.
- Through-hole package for all the components.
- . \bullet DRC rule: Minimum track width and spacing - 10 mils, minimum via hole - 10 mils.



3 Design schematics and layout


Schematic of the Voltage controlled oscillator



Circuit schematic

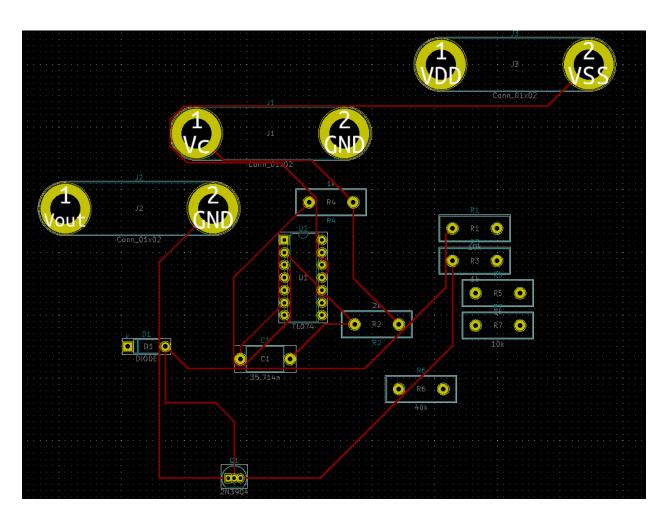
• Using the schematic I have generated a netlist to start PCB after checking for errors.






PCB layout Top layer



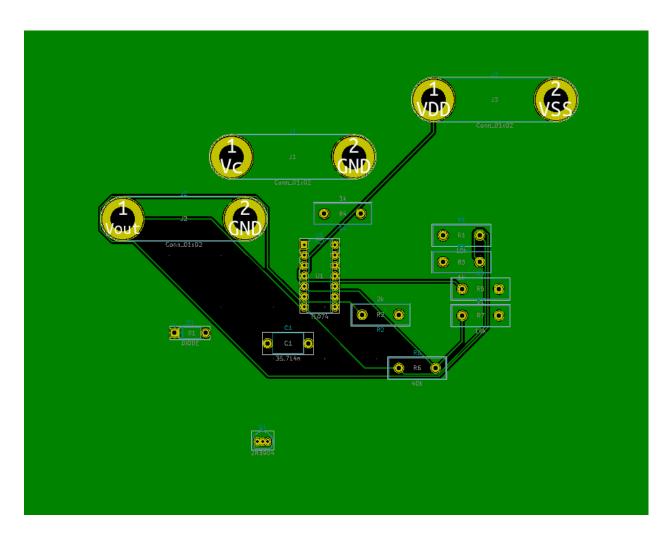

PCB layout Bottom layer




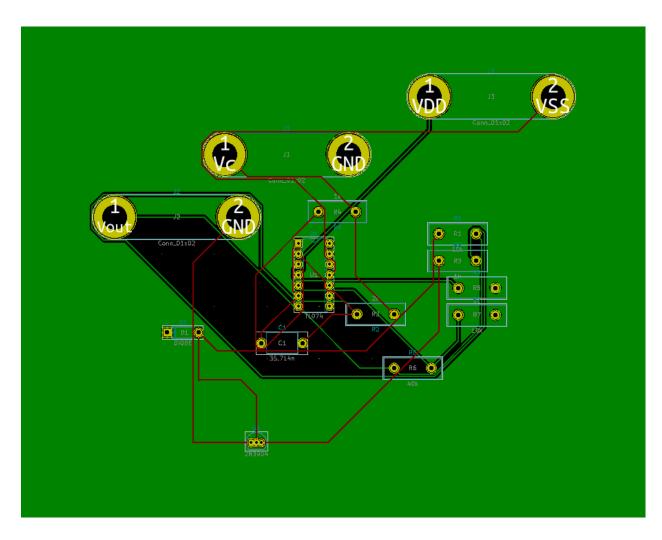

PCB layout Both layer



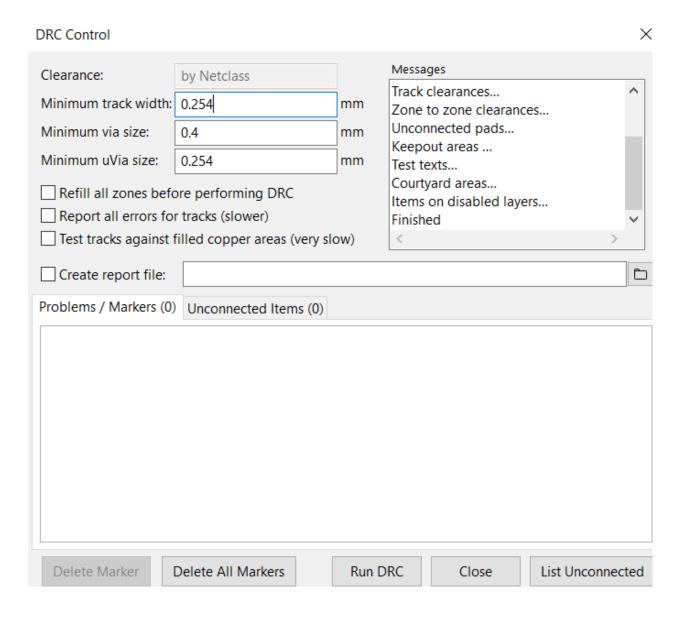PCB minimum parameters for error checking






PCB DRC Report




PCB DRC Report



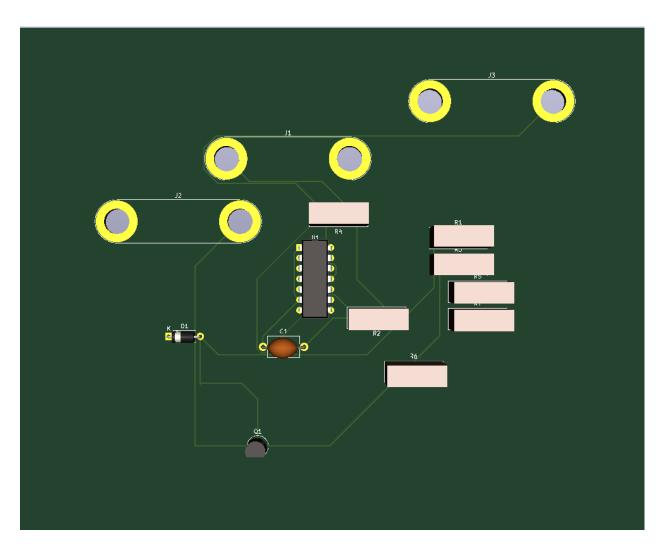


PCB 3d view Top layer



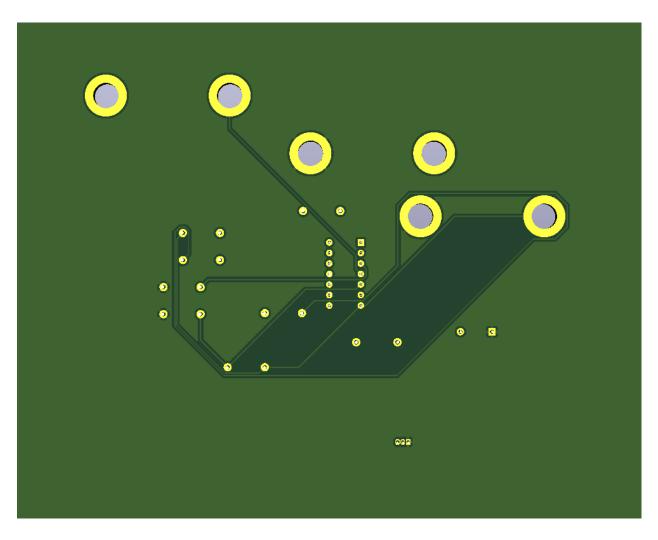


PCB 3d view Bottom layer



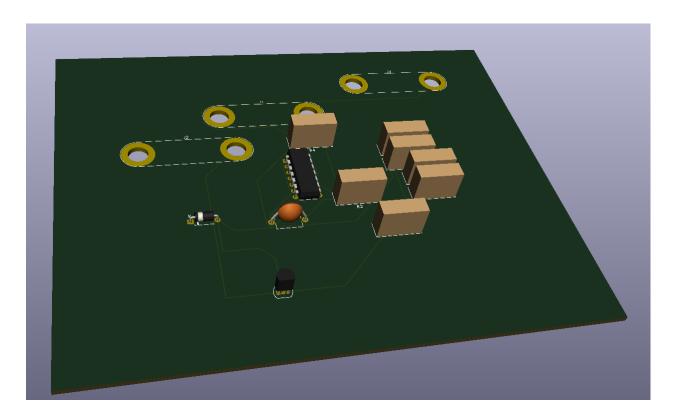

PCB 3d view



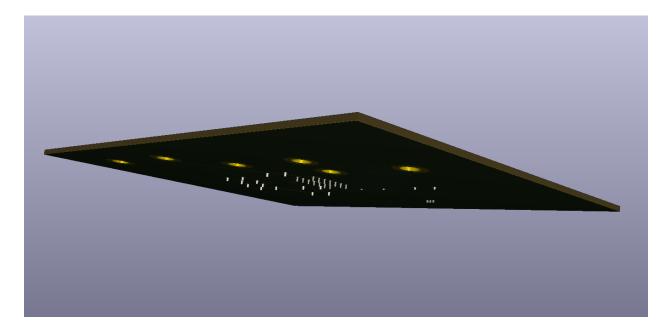

PCB 3d view



Mark