

Analog Lab (EE2401)

Experiment 8: Signal strength detector

EE19BTECH11041,
Srijith Reddy Pakala
Department of Electrical Engineering
IIT Hyderabad


April 15, 2021

1 Aim

our aim here is to design a circuit that can detect strength of a signal using op-amp and diodes.

2 Problem statement

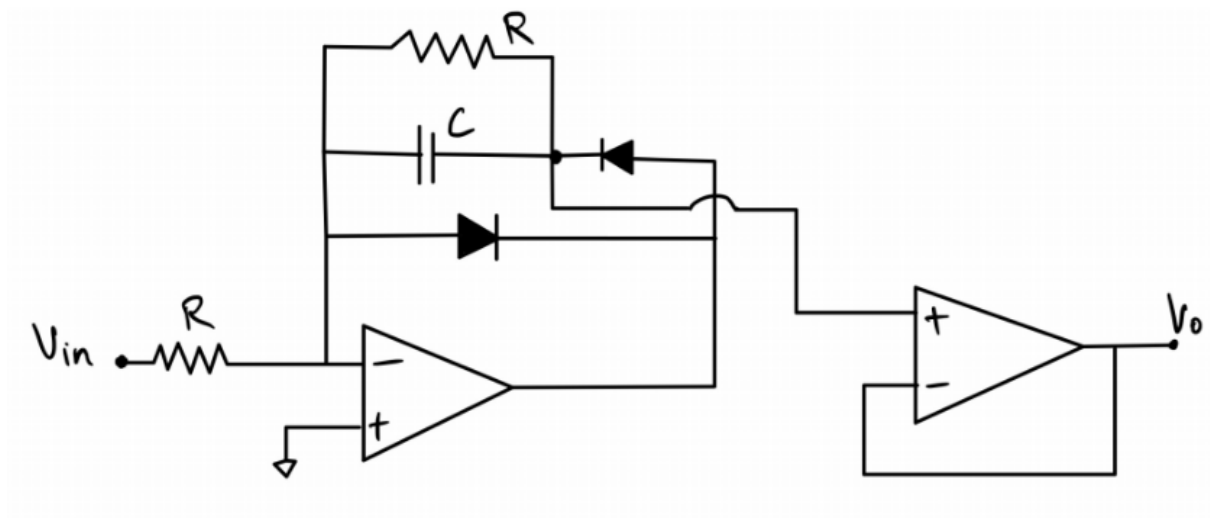1. Find the frequency components (till third harmonic) of a half-wave rectified sinusoidal signal.
2. The following circuit implements a half-wave rectifier with first-order filter to give an output corresponding to the input signal strength (rms).



- . • Input frequency: 0.1 kHz -5 kHz
- . • Choose RC to reject the lowest input frequency
- . • LF347 opamp with +5V/-5V dual supply
- . • Diode 1N4148

Plot input amplitude vs average V_o for 0.1 kHz, 2.5 kHz and 5 kHz. Vary input amplitude from 0 to 5 V. Also submit a transient plot at 2.5 V amplitude for 0.1 kHz and 5 kHz.

Submit the following:

- Testbench snapshot, output plots
- Hand calculation
- Any unusual observation along-with comments

The Fourier series of a periodic function $f(x)$ of period T is

$$f(x) = \frac{a_0}{2} + \sum_{k=1}^{\infty} a_k \cos \frac{2\pi kx}{T} + \sum_{k=1}^{\infty} b_k \sin \frac{2\pi kx}{T}$$

$$a_k = \frac{2}{T} \int_0^T f(x) \cos \frac{2\pi kx}{T} dx$$

$$b_k = \frac{2}{T} \int_0^T f(x) \sin \frac{2\pi kx}{T} dx$$

- Now we will use this equation to find frequency components (until third harmonic) for half-wave rectified sinusoidal signal.

$$a_0 = \frac{2}{T} \int_0^{T/2} \sin \frac{2\pi kx}{T} dx = \frac{\cos(0) - \cos(\pi)}{\pi} = \frac{2}{\pi}, \quad a_1 = \frac{2}{T} \int_0^{T/2} \sin \frac{2\pi kx}{T} \cos \frac{2\pi kx}{T} dx = 0$$


$$a_2 = \frac{2}{T} \int_0^{T/2} \sin \frac{2\pi kx}{T} \cos \frac{4\pi kx}{T} dx = \frac{-2}{3\pi}, \quad a_3 = \frac{2}{T} \int_0^{T/2} \sin \frac{2\pi kx}{T} \cos \frac{6\pi kx}{T} dx = 0$$

$$b_1 = \frac{2}{T} \int_0^{T/2} \sin \frac{2\pi kx}{T} \sin \frac{2\pi kx}{T} dx = \frac{1}{2}$$

$$b_2 = \frac{2}{T} \int_0^{T/2} \sin \frac{2\pi kx}{T} \sin \frac{4\pi kx}{T} dx = 0$$

$$b_3 = \frac{2}{T} \int_0^{T/2} \sin \frac{2\pi kx}{T} \sin \frac{6\pi kx}{T} dx = 0$$
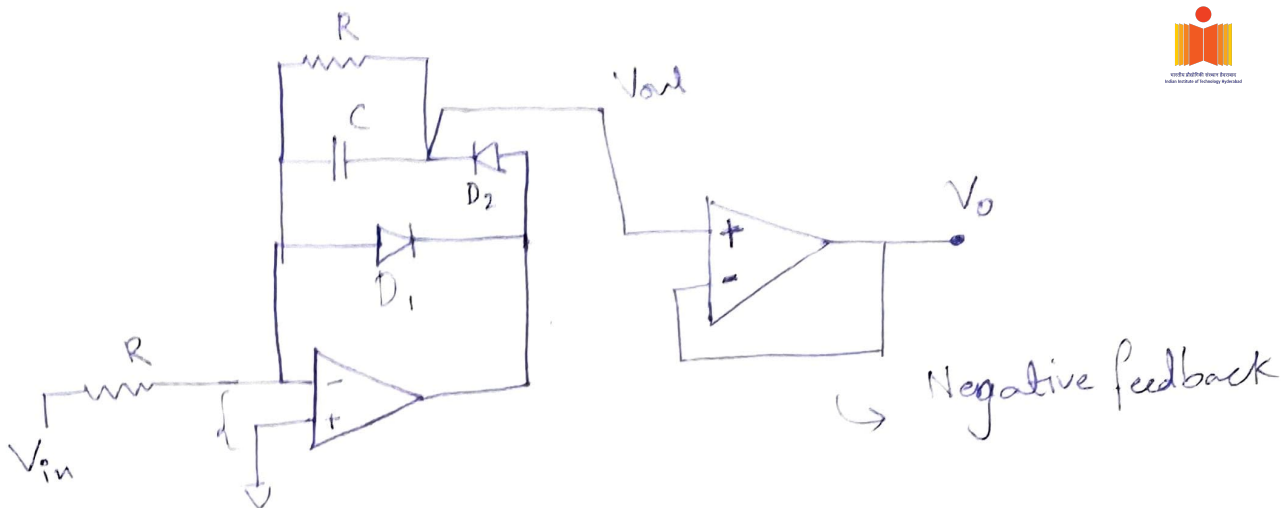
$$f(x) = \frac{1}{\pi} + \frac{-2}{3\pi} \cos \frac{4\pi x}{T} + \frac{1}{2} \sin \frac{2\pi x}{T} + \dots$$



when $V_{in} > 0$.

then D_1 is forward biased.

$$\Rightarrow V_{out} = 0$$

when $V_{in} < 0$

D_1 is reversed biased and D_2 is forward biased and is in negative feedback.

Due to virtual short.

$$\frac{V_{in} - 0}{R} = \frac{0 - V_{out}}{R} \cdot \frac{1}{1 + sRC}$$

$$\Rightarrow V_{out} = -\frac{V_{in}}{1 + sRC}$$

Therefore it essentially acts like a lowpass.

with $f_0 = \frac{1}{2\pi RC}$.

Here input range is 0.1 - 5 KHz.

$$\Rightarrow \frac{1}{2\pi RC} < 0.1 \text{ KHz to have only dc}$$


component of input. i.e. $\frac{1}{\pi}$ of component.

Now the capacitor will get charged and as a result In steady state the output itself will be maintained at $\frac{1}{\pi}$.

and since when $V_{in} > 0$, there is no current through capacitor so, $\frac{1}{\pi}$ will be maintained.

Op-amp 2 is just a negative feedback with output same as input.

Schematic of signal strength detector

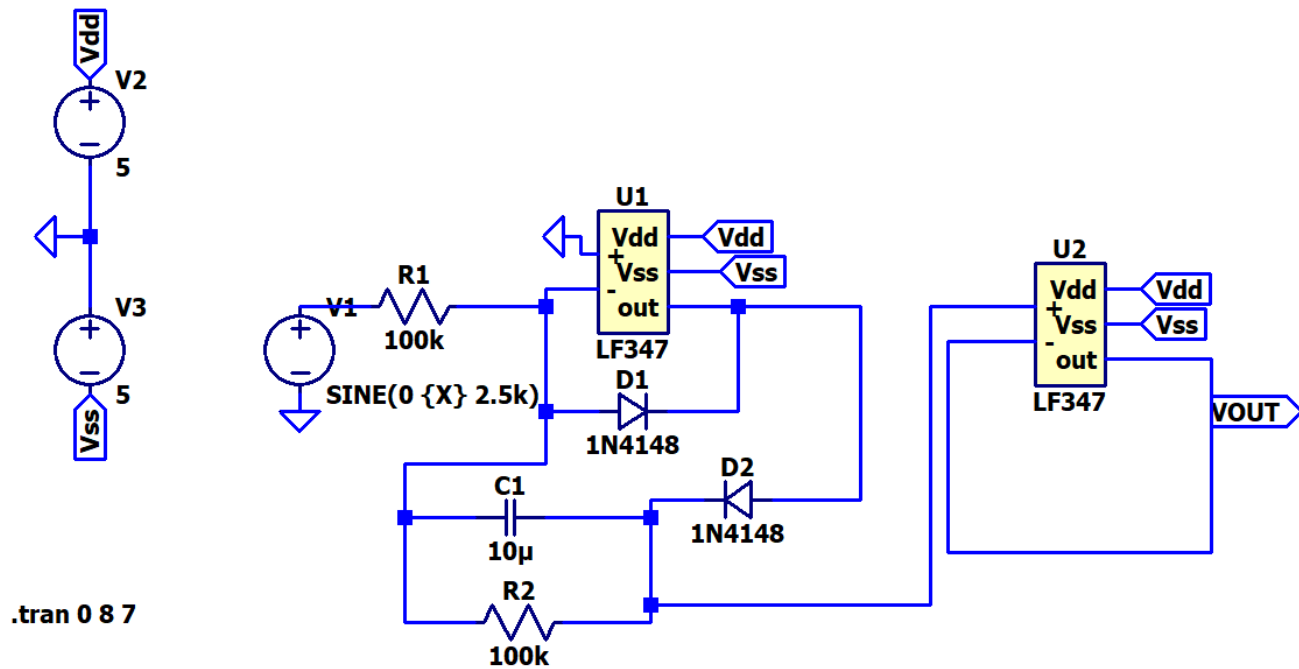

.tran 0 8 7

.step param X 0 5 0.25

.meas Vo AVG V(vout)


circuit schematic

.tran 0 8 7


.step param X 0 5 0.25

.meas Vo AVG V(vout)


Input amplitude vs average V_o

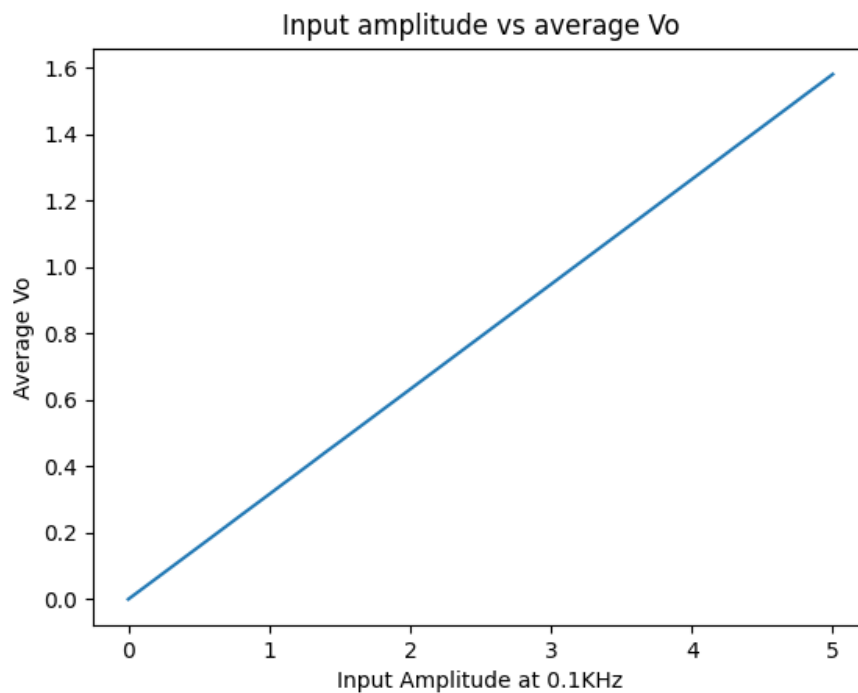


Input amplitude vs average V_o at 0.1KHz

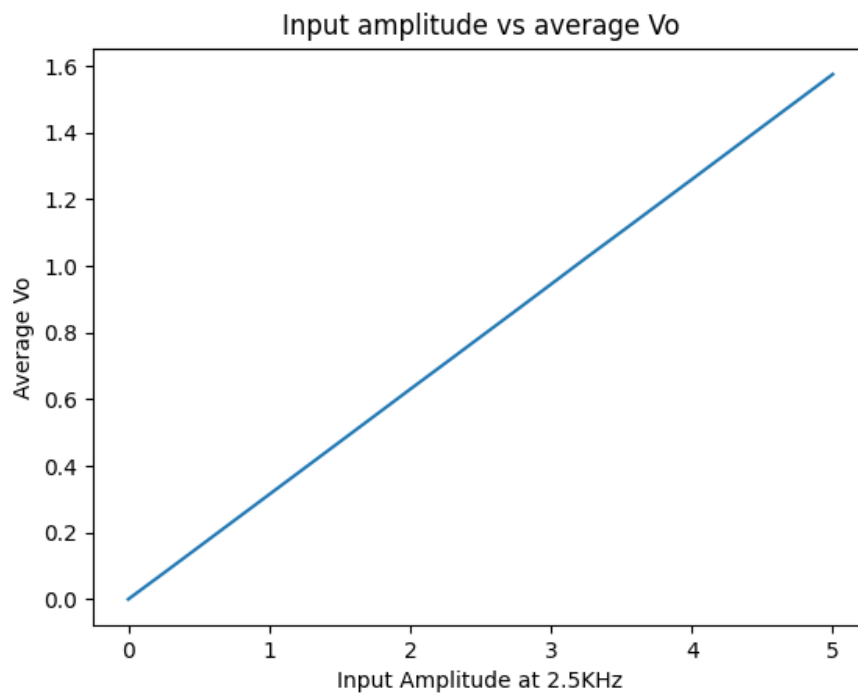

Input amplitude vs average V_o at 2.5KHz

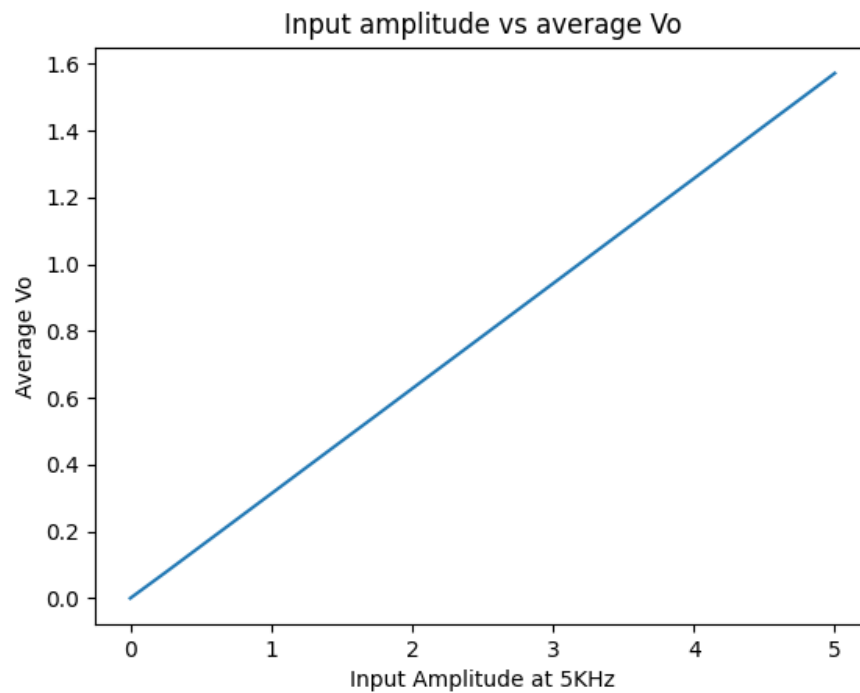



Input amplitude vs average Vo at 5KHz

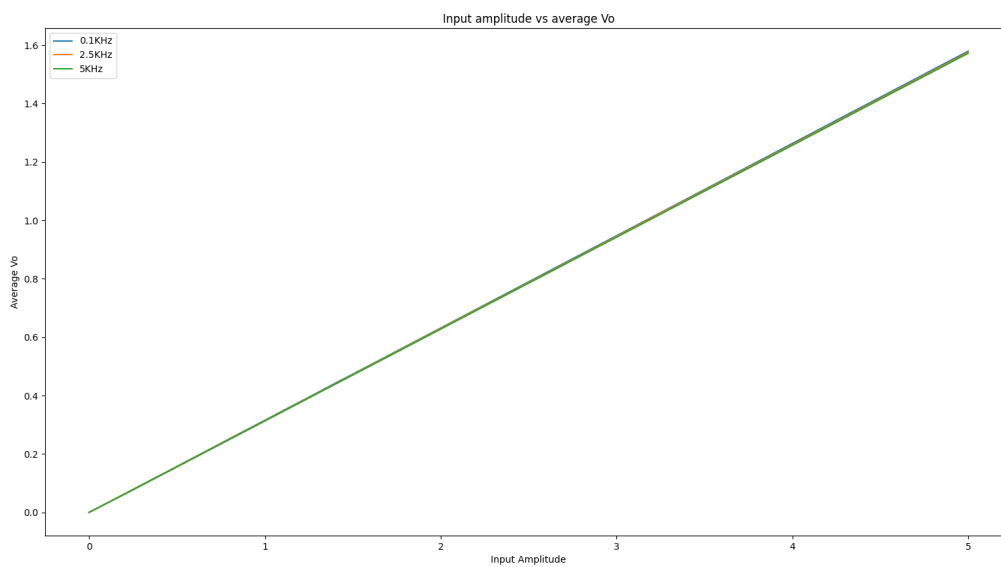


Input amplitude vs average Vo at 0.1KHz,2.5KHz,5KHz

- As we can see that the average Vo is approximately $\frac{A}{\pi}$ where A is the input amplitude as expected.

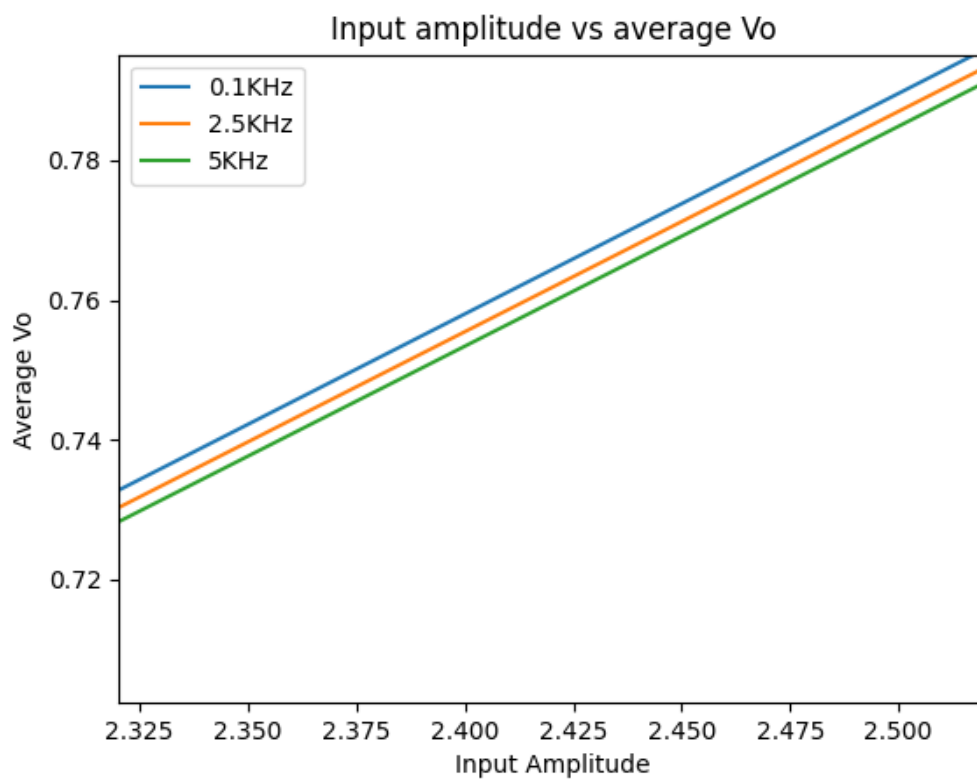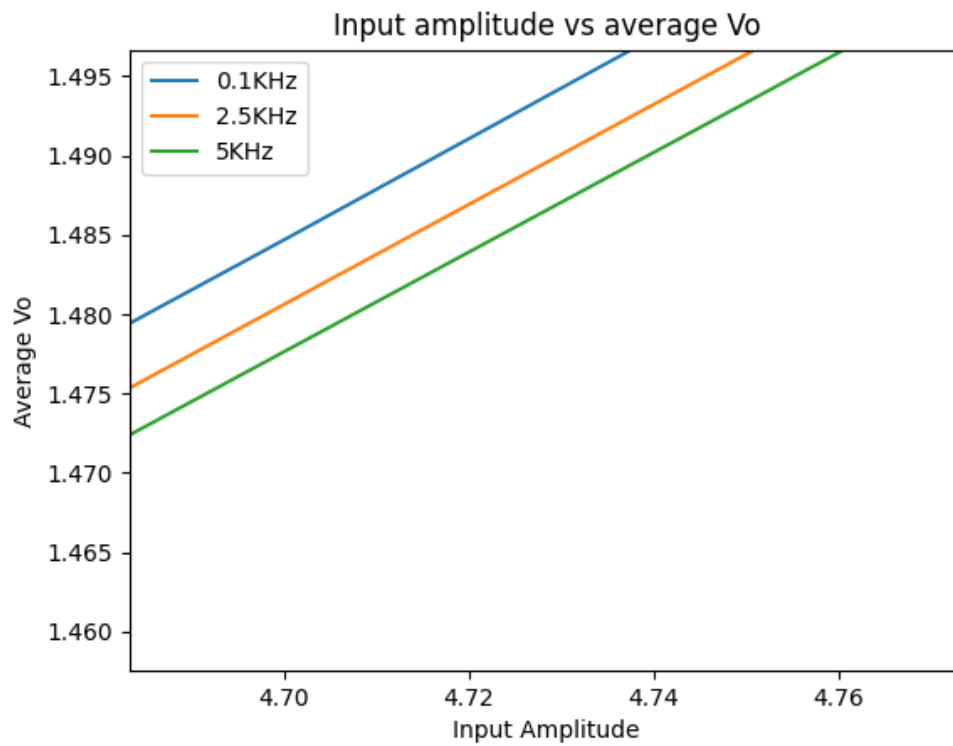Input amplitude vs average V_o at closely




Output time domain at 0.1KHz

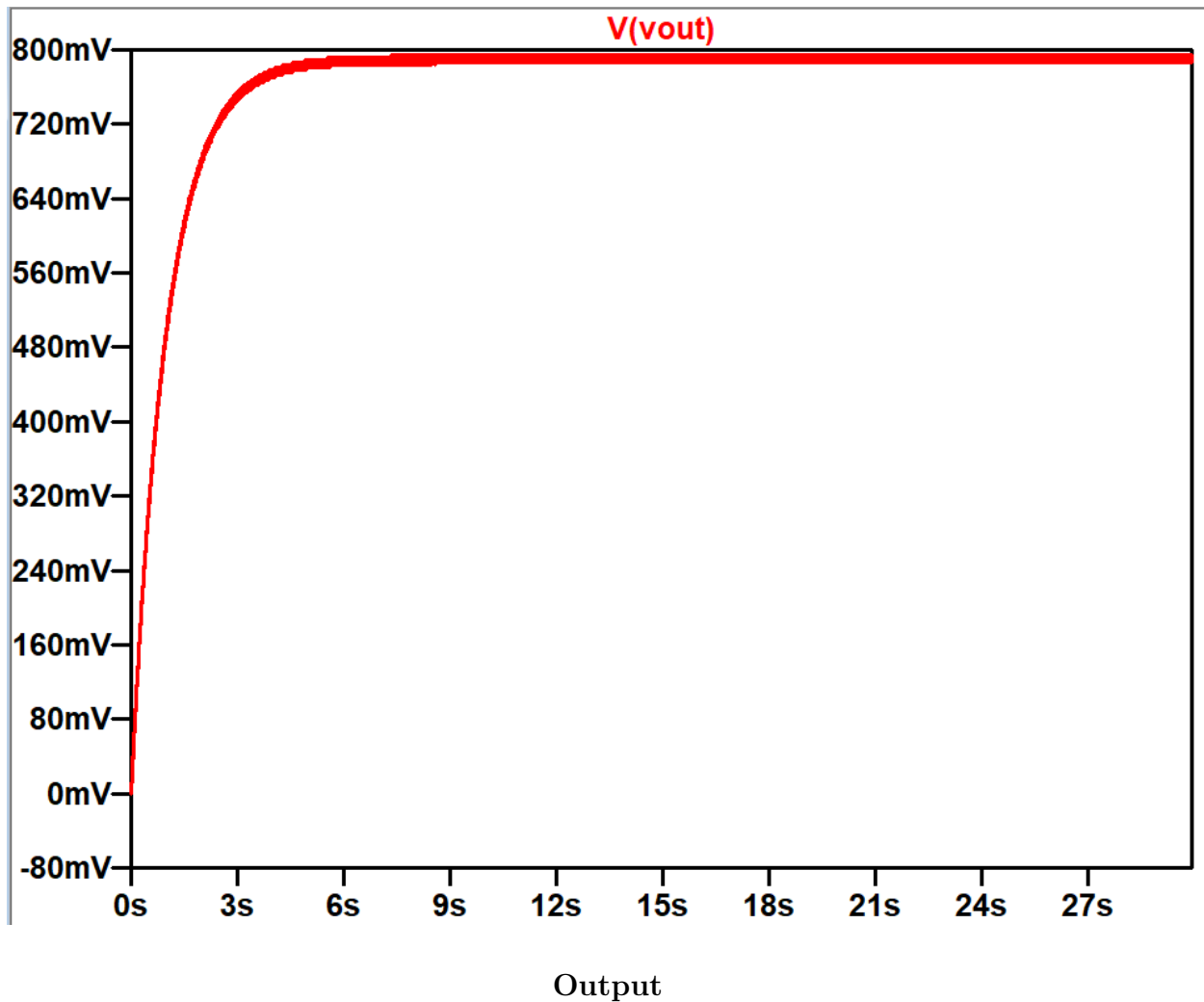

- The input is sinusoid with 0.1KHz and Amplitude 2.5V.
- The output here increases until some transient period and then achieves steady state around 800mV.
- The average output matches with the expected value i.e. $\frac{2.5}{\pi}$.

Output time domain at 5KHz

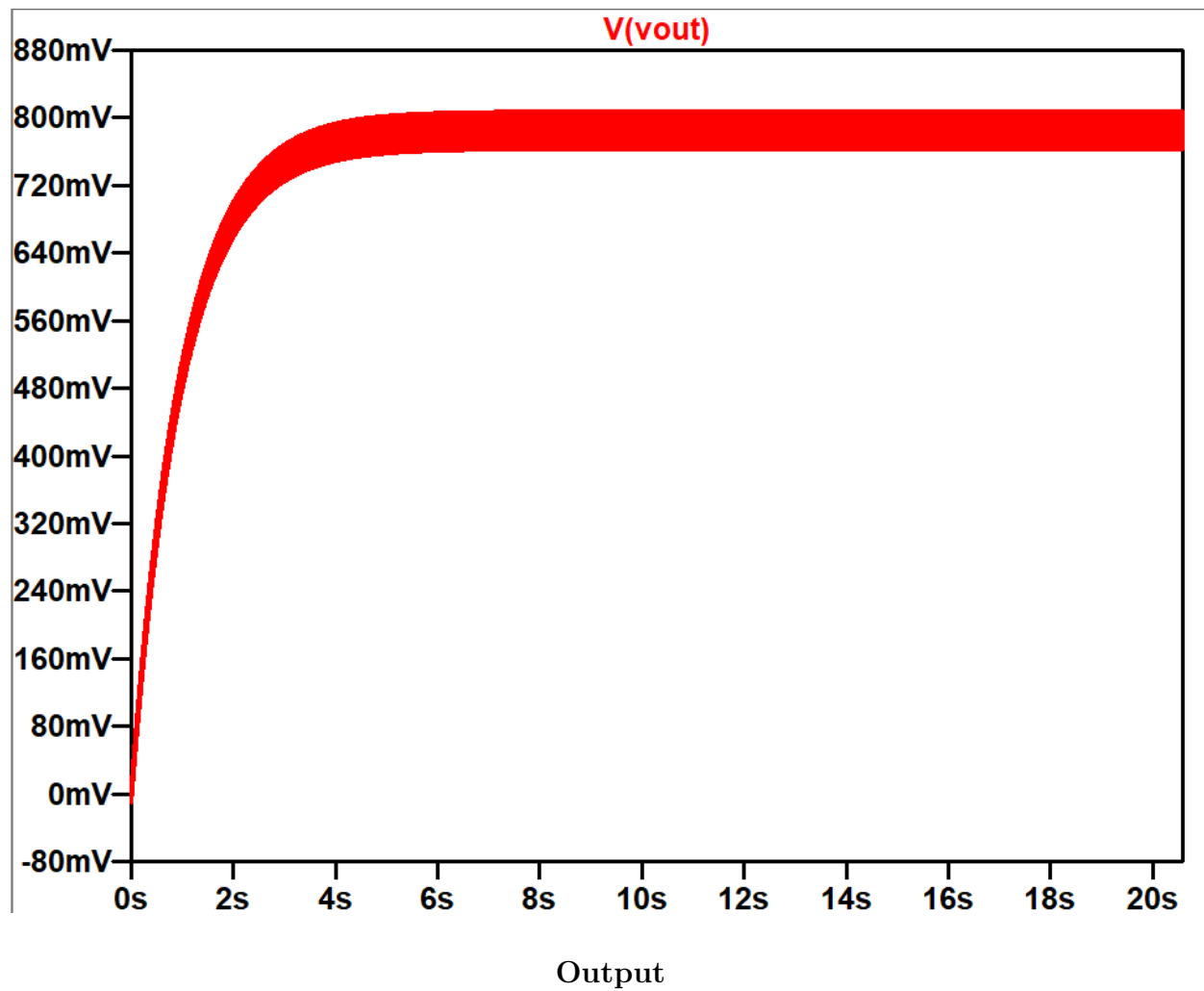

- The output at 5KHz is similar to the one at 0.1KHz as expected but around 780mV.

Thank
you